

CSED311 Lab1: RTL Design

Hyunuk Cho

gusdnr9779@postech.ac.kr


Contact the TAs at csted311-ta@postech.ac.kr

Contents

- Combinational logic
- Register-Transfer Level
- Finite State Machine
- Assignments
 - Combinational logic (ALU)
 - FSM (vending machine)

Combinational logic

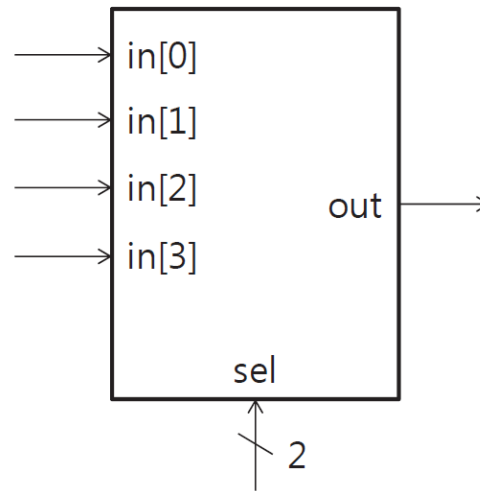- Represents Boolean function (time(clk)-independent)
- Output is a function of inputs only
- $\text{output} = f(\text{input})$
- Example: 4-to-1 mux



[3:0]in	sel	out
2'bxxx0	2'b00	0
2'bxxx1	2'b00	1
2'bxx0x	2'b01	0
2'bxx1x	2'b01	1
2'bx0xx	2'b10	0
2'bx1xx	2'b10	1
2'b0xxx	2'b11	0
2'b1xxx	2'b11	1


Combinational logic

- Implementation with Verilog (mux)
 - If you use “always”, simply giving “(*)” as the sensitivity list is equivalent to the code below

Using Assign	Using Always
<pre>module mux(in, sel, out); input [3:0] in; input [1:0] sel; output out; assign out = (sel == 2'b00) ? in[0] : (sel == 2'b01) ? in[1] : (sel == 2'b10) ? in[2] : in[3]; endmodule</pre>	<pre>module mux(in, sel, out); input [3:0] in; input [1:0] sel; output out; reg out; always @ (sel or in) begin if (sel == 2'b00) out = in[0]; else if (sel == 2'b01) out = in[1]; else if (sel == 2'b10) out = in[2]; else out = in[3]; end endmodule</pre>

Combinational logic

■ RTL schematic

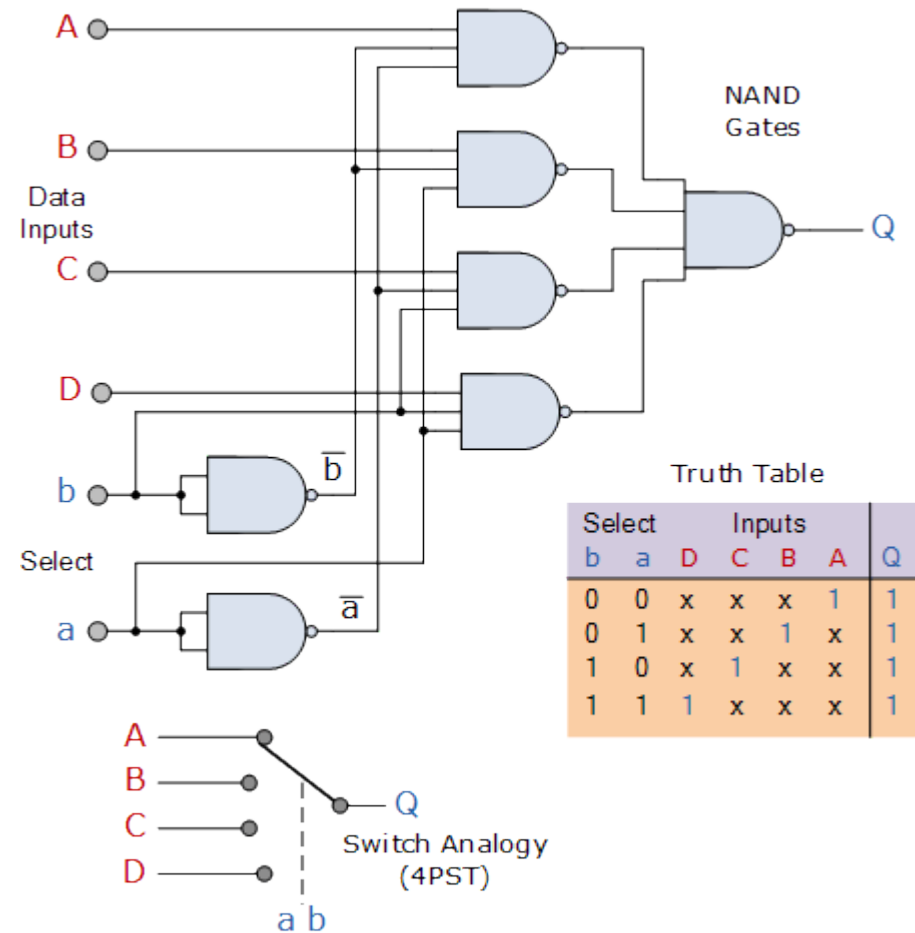


Register-Transfer Level

- The design method to implement a **synchronous circuit** with an HDL (Hardware Description Language)
- Synchronous circuit consists of:
 - **Register**: a memory element synchronized by the clock signal
 - **Combinational logic**: logical function

RTL - example

■ Toggler example

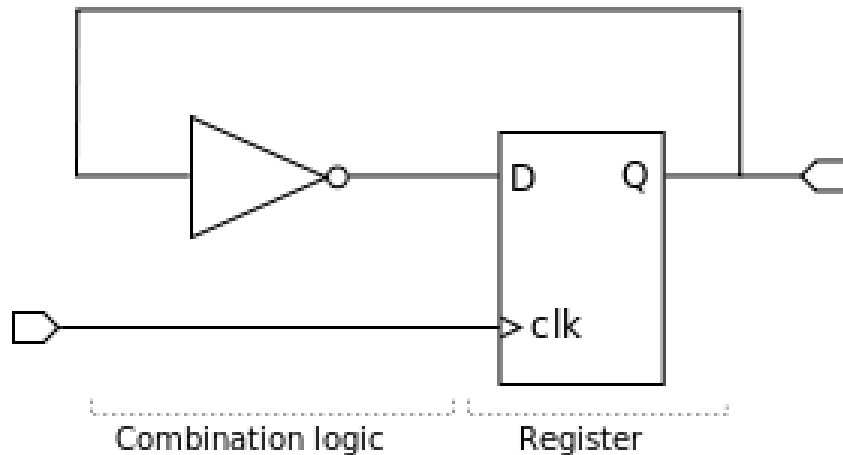

<Fig 1. "Register transfer level - example toggler" (Register-transfer level, Wikipedia, https://en.wikipedia.org/wiki/Register-transfer_level)>

```
module toggler(input clk, output out);  
    reg state;  
    wire comb;  
  
    assign comb = ~state;  
    assign out = state;  
  
    initial begin  
        state <= 0;  
    end  
  
    always @(posedge clk) begin  
        state <= comb;  
    end  
endmodule
```


Finite State Machine (FSM)

- Moore Machine
- Mealy Machine

Finite State Machine (FSM)


- Moore Machine

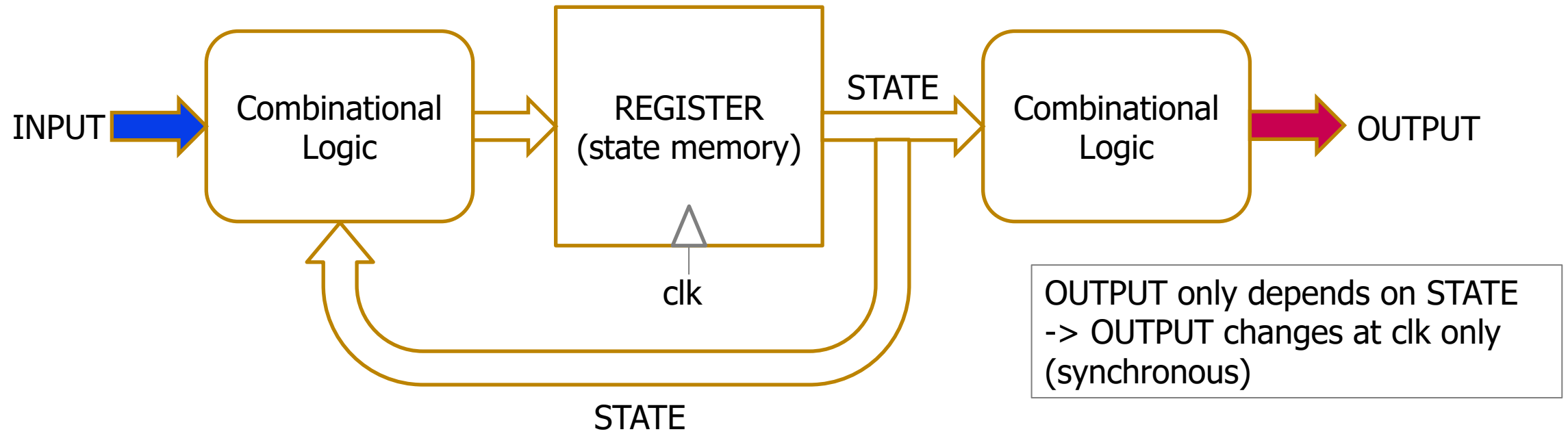- Outputs only depend on the current state.




Finite State Machine (FSM)

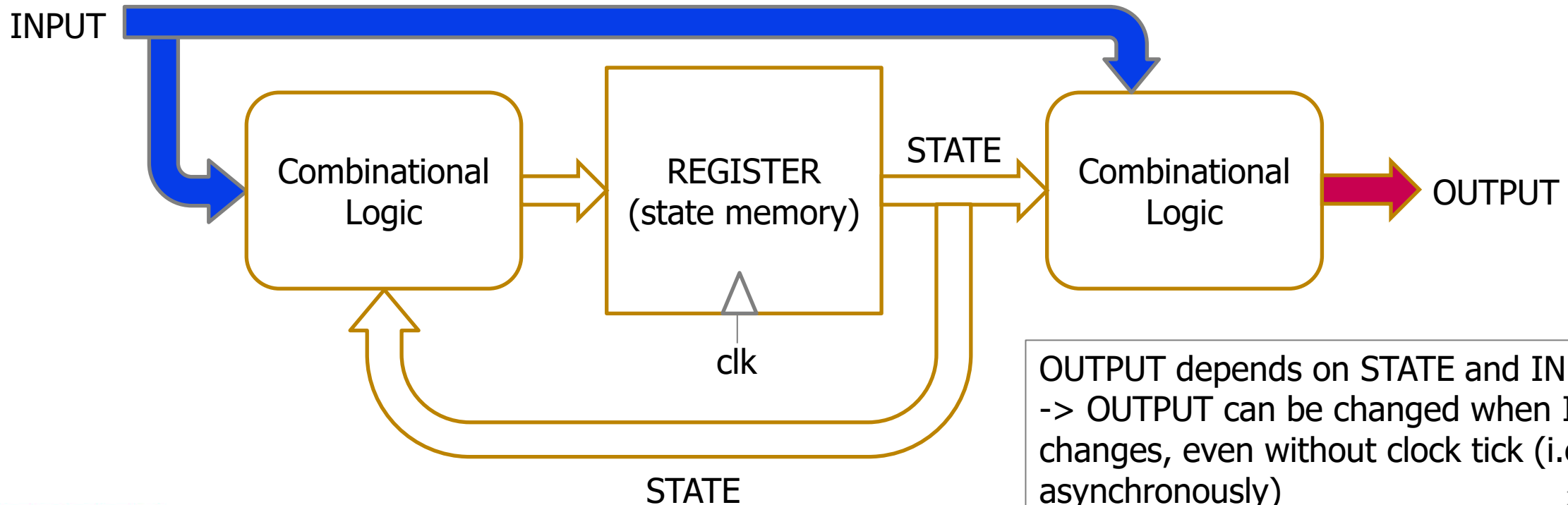- Mealy Machine
 - Outputs depend on the current state and the current inputs




Finite State Machine (FSM)

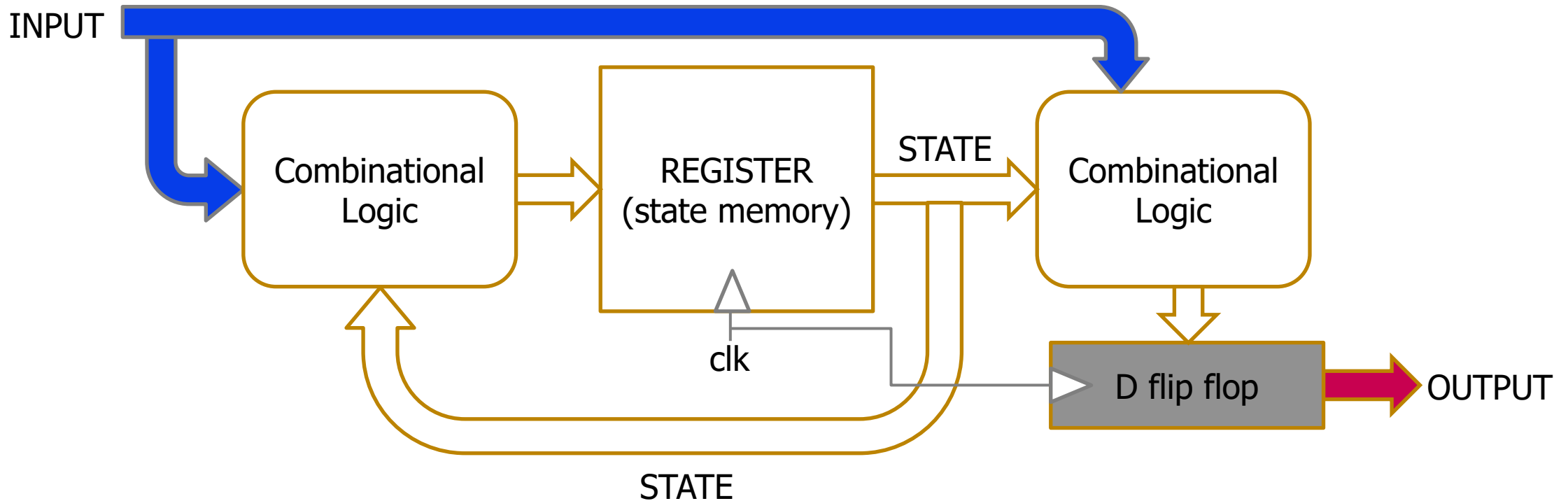- Mealy Machine
 - Mealy Machine can be made synchronous




FSM Code Structure

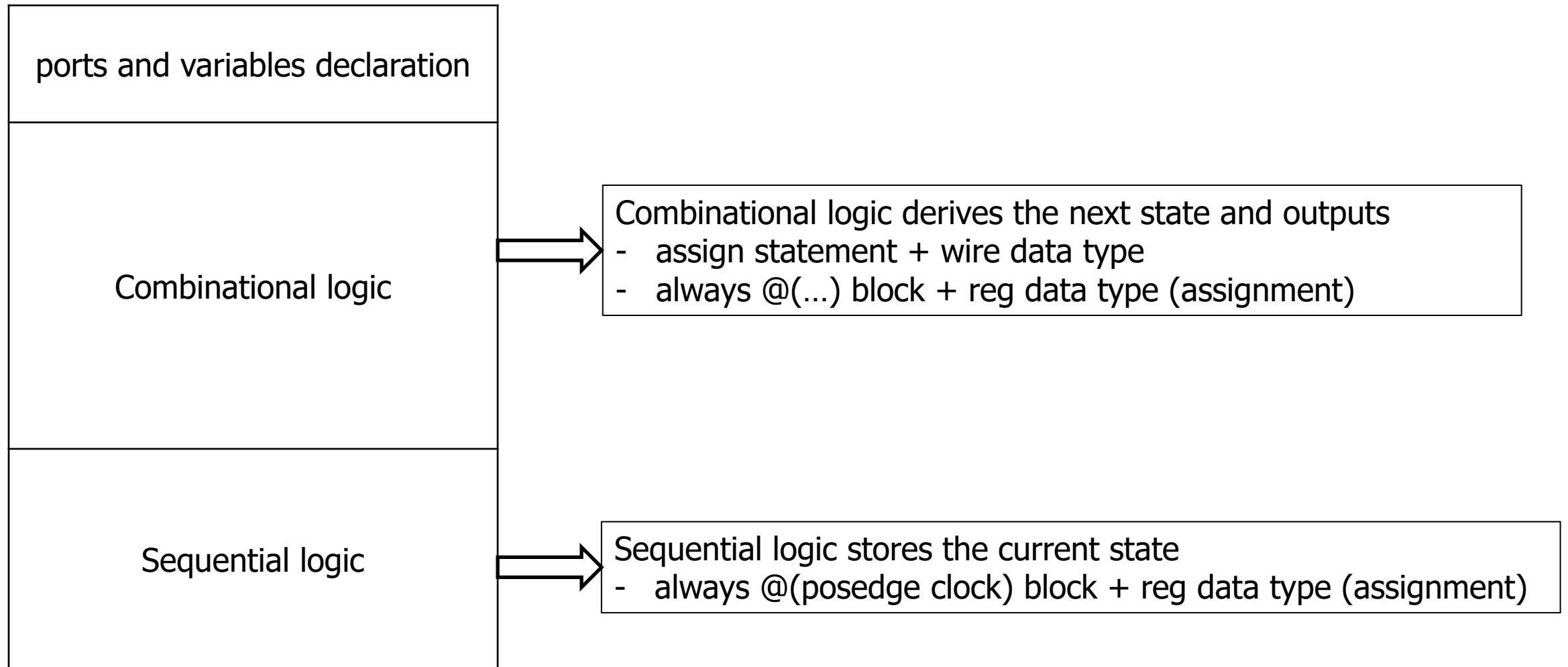

FSM Code Structure

❖ Example: Mealy Machine

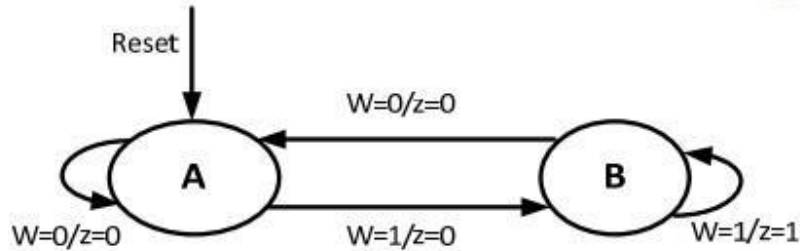

Output: reg

Example: Reduce 1's

Given a sequence of 0s and 1s, *change the first 1 of consecutive 1s into 0*

Examples:

000011100 -> 000001100

010101010 -> 000000000

011001100 -> 001000100

z is output and z is in combinational logic part
-> asynchronous Mealy Machine

NS & Output
Calculation


CS
Calculation

```
module mealy (Clock, w, Resetn, z);
  input Clock, w, Resetn ;
  output reg z ;
  reg CS, NS;
  parameter A = 1'b0, B = 1'b1;
  always @(w, CS)
    case (CS)
      A: if (w == 0)
          begin
            NS = A; z = 0;
          end
        else
          begin
            NS = B; z = 0;
          end
      B: if (w == 0)
          begin
            NS = A; z = 0;
          end
        else
          begin
            NS = B; z = 1;
          end
    endcase
  always @(posedge Clock, negedge Resetn)
    if (Resetn == 0)
      CS <= A;
    else
      CS <= NS;
endmodule
```

Combinational
(Blocking)

Sequential
(Non-Blocking)

FSM Code Structure

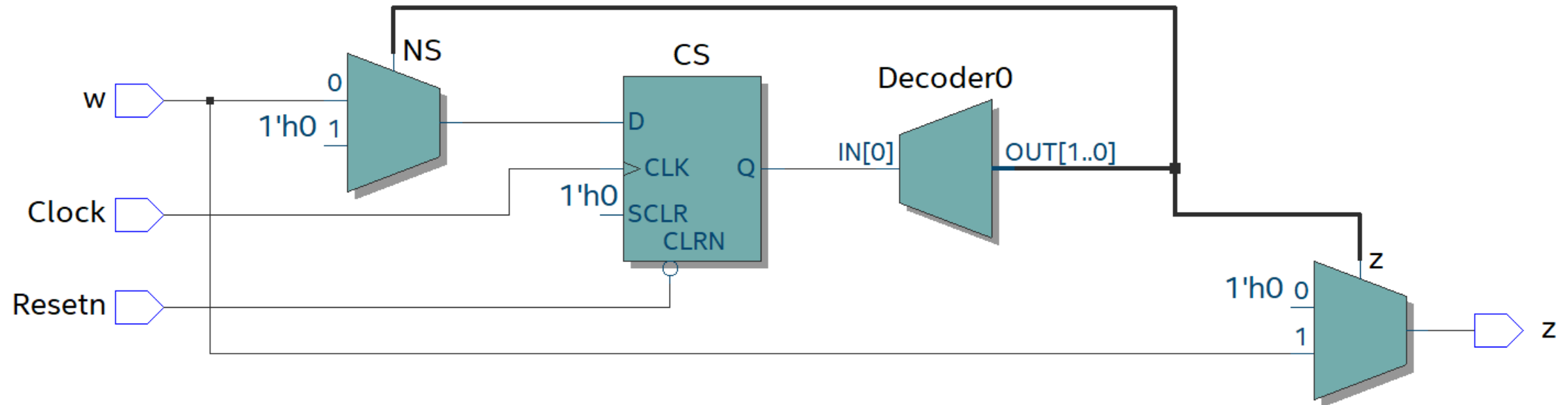

Assignment 1.a

- Implement ALU (Arithmetic Logic Unit) in Verilog
- A skeleton code and testbench will be provided
 - Lab1/ALU/*
- Input: (A, B, FuncCode)
 - A: left operand (16-bit signed binary)
 - B: right operand (16-bit signed binary)
 - FuncCode: operator (4-bit binary)
- Output: (C, OverflowFlag)
 - C: operation result (16-bit signed binary)
 - OverflowFlag: overflow flag (1-bit binary)

Assignment 1.a (cont'd)

■ ALU operations

FuncCode	Operation	Comment
0000	$A + B$	Signed Addition
0001	$A - B$	Signed Subtraction
0010	A	Identity
0011	$\sim A$	Bitwise NOT
0100	$A \& B$	Bitwise AND
0101	$A B$	Bitwise OR
0110	$\sim(A \& B)$	Bitwise NAND
0111	$\sim(A B)$	Bitwise NOR

FuncCode	Operation	Comment
1000	$A \oplus B$	Bitwise XOR
1001	$\sim(A \oplus B)$	Bitwise XNOR
1010	$A \ll 1$	Logical Left Shift
1011	$A \gg 1$	Logical Right Shift
1100	$A \lll 1$	Arithmetic Left Shift
1101	$A \ggg 1$	Arithmetic Right Shift
1110	$\sim A + 1$	Two's Complement
1111	0	Zero

Assignment 1.a (cont'd)

- Overflow detection
- For addition and subtraction, you should detect overflow and set the flag.

Overflow Flag	Singed Addition	Signed Subtraction
0	Correct Result	Correct Result
1	Wrong Result	Wrong Result

- For other operations, OverflowFlag is always zero.

Assignment 1.b

- Implement a simple vending machine RTL in Verilog
 - A simple Finite State Machine (FSM)
- Your vending machine should cover all use-cases (in the next slides)
- A skeleton code and testbench will be provided
 - Lab1/vending_machine/

Assignment 1.b (cont'd)

■ Vending machine interface

INPUT		
Signal	Description	Number of bit(s)
i_input_coin	Insert Coin	1 for each type of coins
i_select_item	Select Item	1 for each type of items
i_return_trigger	Return change	1
clk	clock	1
reset_n	reset	1

OUTPUT		
Signal	Description	Number of bit(s)
o_output_item	Indicate dispensed items	1 for each type of items
o_available_item	Indicate item availability	1 for each type of item
o_return_coin	Indicate type of coin (change)	1 for each type of coins

Assignment 1.b (cont'd)

■ Vending machine use-case

Assumption: infinite item, change

Sequence

1. Insert money (available money unit: 100, 500, 1000 won) and initialize waiting time(=100)
 2. Vending machine shows all available items where (item cost \leq current money)
 - 2.a. decrease waiting time(-1)
 - 3.a. Insert money within the waiting time
 - 3.a.1. Go to 2 and initialize waiting time(=100)
 - 3.b. Select an item within the waiting time
 - 3.b.a. Case1: the item is available
 - 3.b.a.1. The item is dispensed
 - 3.b.a.2. Go to 2 and initialize waiting time(=100)
 - 3.b.b. Case 2: the item is unavailable
 - 3.b.b.1. Nothing happens. Waiting time is not reset.
 - 3.c. No input within the waiting time
 - 3.c.1 Return changes
- a*. Whenever press the return button
- a*.1. Return changes
 - a*.2. Go to 1

Assignment 1.b (cont'd)

- If your modelsim is not displaying the output of \$display or \$monitor, then try using vending_machine_tb_f.v. (output will be written to output.txt)
- If your simulation keeps running, the testbench module is waiting for the output signals. (o_output_item or o_return_coin)
- If your vending machine code passes all tests, you will get the message “Passed = 23, Failed = 0”

Evaluation Criteria (Source code)

- ALU
 - Number of tests passed from the shared TB
- Vending machine
 - Number of tests passed from the shared TB as well as additional TB not shared
 - Modularization
 - Your implementation should include at least two modules
 - Using modules lowers implementation complexity
 - Similar to the functions in other programming languages
 - It would be helpful to practice before implementing CPUs
 - Understanding of combinational/sequential logic
 - E.g.) Appropriate use of blocking/non blocking assignment

Evaluation Criteria (Report)

- You can write report in Korean or English
- Report should include (1) introduction, (2) design, (3) implementation, (4) discussion, and (5) conclusion
- ALU
 - Report not evaluated, source code only
- Vending machine
 - Combinational logic design and implementation
 - Sequential logic design and implementation
 - FSM type of your design
 - Moore or mealy machine

Assignment tips

- #1:** When modeling sequential logic, use nonblocking assignments.
- #2:** When modeling latches, use nonblocking assignments.
- #3:** When modeling combinational logic with an always block, use blocking assignments.
- #4:** Do not mix blocking and nonblocking assignments in the same always block.
- #5:** Do not make assignments to the same variable from more than one always block.
- #6:** Use \$strobe to display values that have been assigned using nonblocking assignments.
- #7:** Do not make assignments using #0 delays.

Assignment Submission

- Submit your assignment to LMS with filename:
 - Lab1_{TeamID}_{StudentID1}_{StudentID2}.pdf
 - PDF file of your report
 - Lab1_{TeamID}_{StudentID1}_{StudentID2}.zip
 - Zip file of your source code (**without testbench**)
 - One directory including two subdirectories (ALU, vending_machine) when unzipped
- Due date
 - ALU (1 week), vending machine (1 week) merged into 2 weeks to help students to distribute time freely
 - Code: **2022. 3. 15 / 09:00 a.m.**
 - Report: **2022. 3. 15 / 23:59 p.m.**

Announcement

- Please check your team in PLMS
 - If you don't send email to TAs until tomorrow (Feb. 29) midnight we will consider you a single-person team
- If you have any question, please post them on the Q&A board in PLMS

Reference

- “Register-transfer level”, Wikipedia, last modified Jan 24, 2019, accessed Mar 03, 2019, https://en.wikipedia.org/wiki/Register-transfer_level
- http://www.sunburst-design.com/papers/CummingsSNUG2000SJ_NBA.pdf